
 


Lab1 – Part 1


One bit data width D flip-flop

 


One bit data width D flip-flop with active low synchronous reset



 
One bit data width D flip-flop with active low synchronous reset and active low enable




D latch with synchronous enable control

 

4-to-1 multiplexer

 

4-bit counter with reset and enable controls

 

Lab1 – Part 3

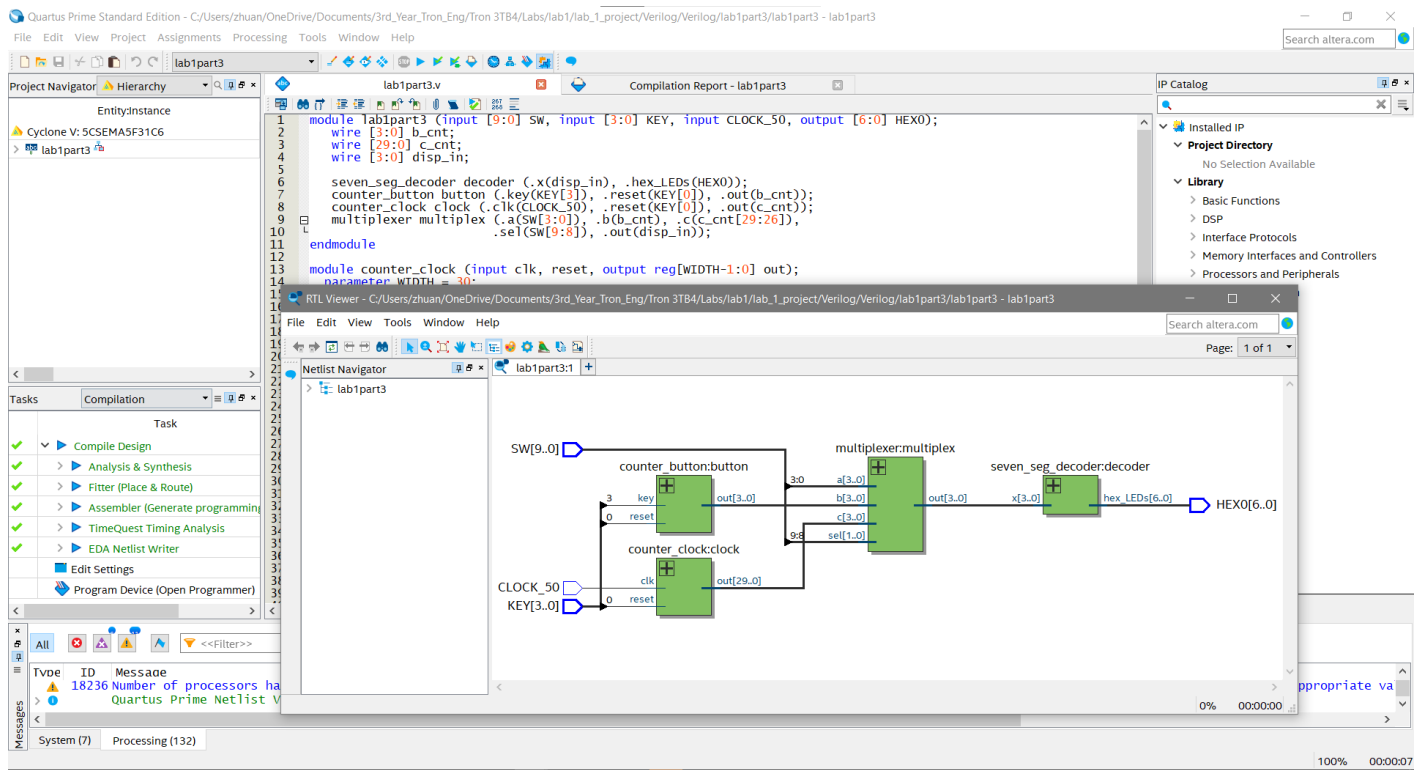


Figure 1: RTL Viewer of Part 3 Compilation – Overview of the Project

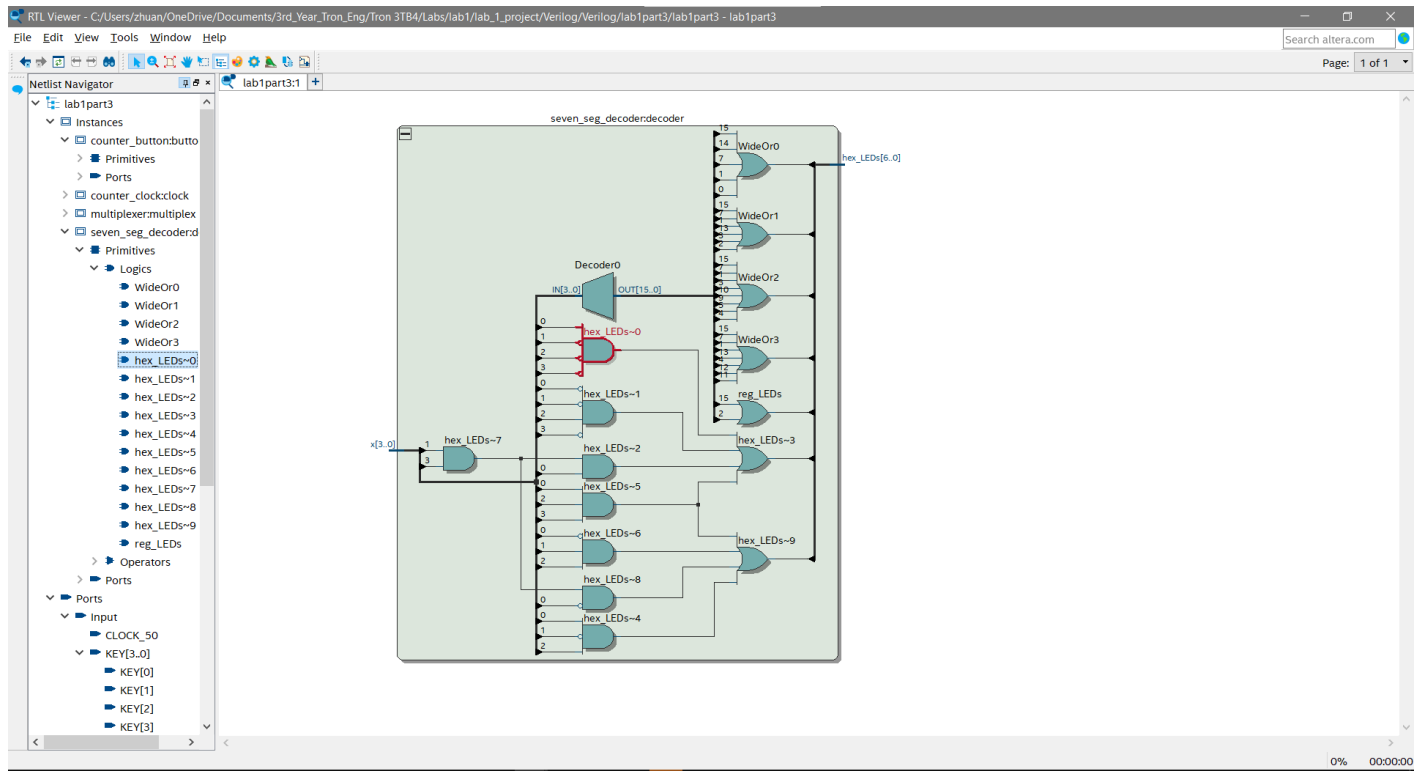


Figure 2: RTL View of Seven-Segment Decoder

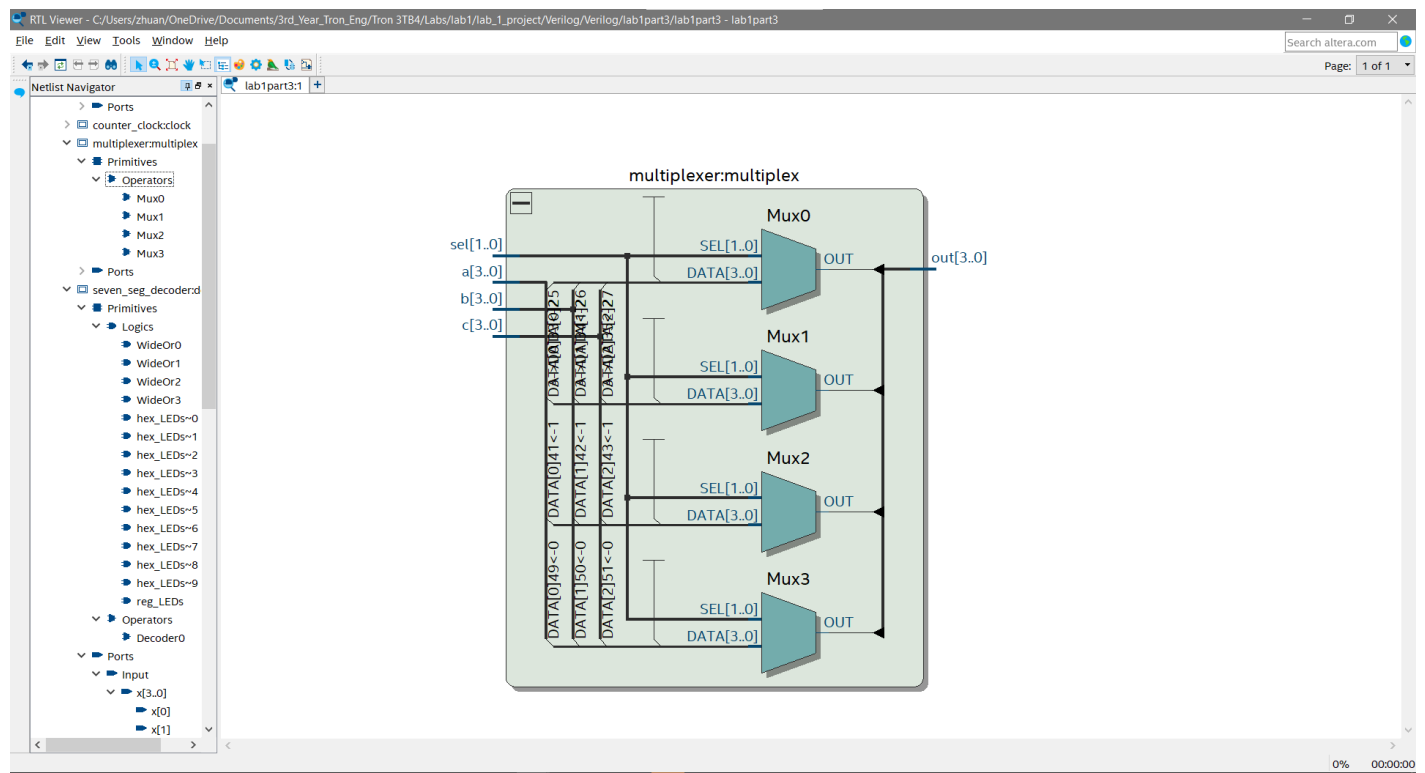


Figure 3: RTL View of the Multiplexer

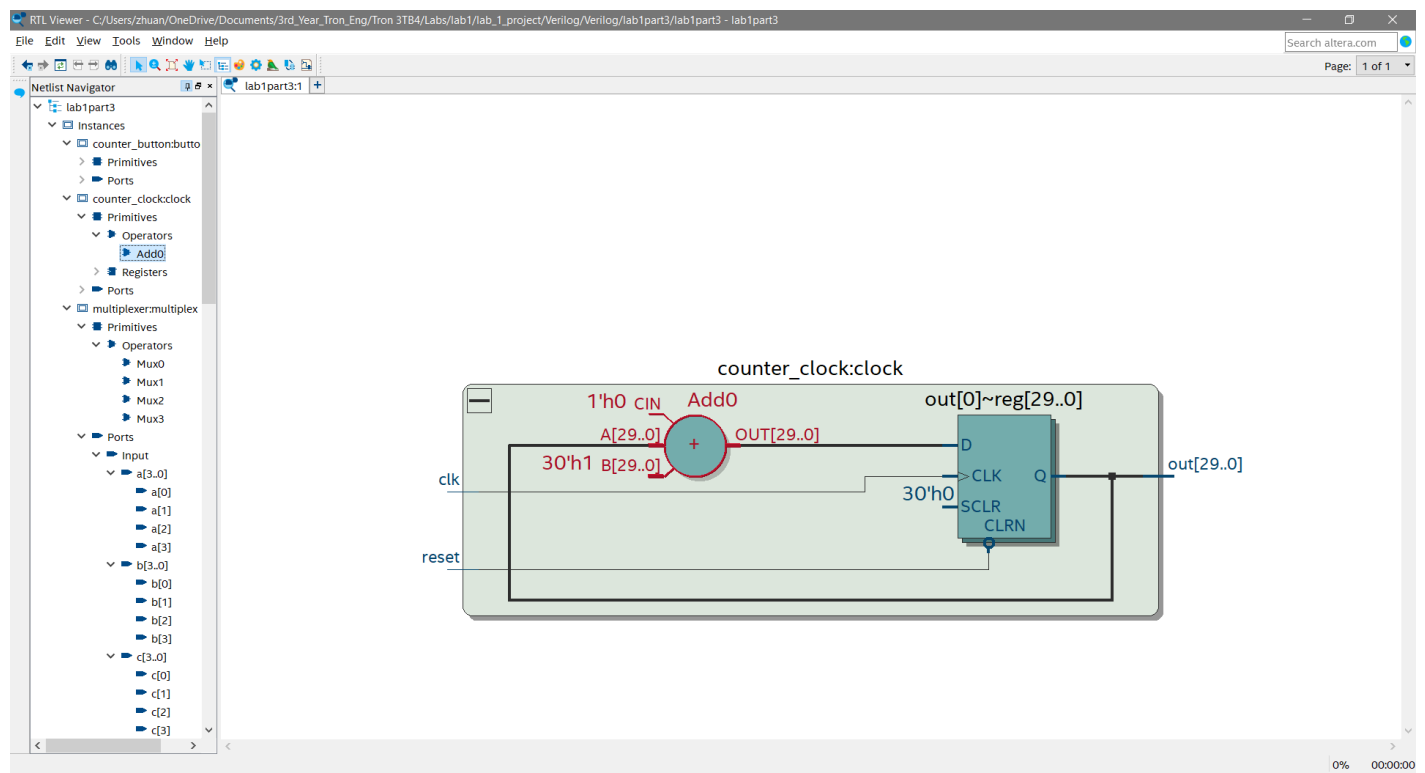


Figure 4: RTL View of the Counter Clock

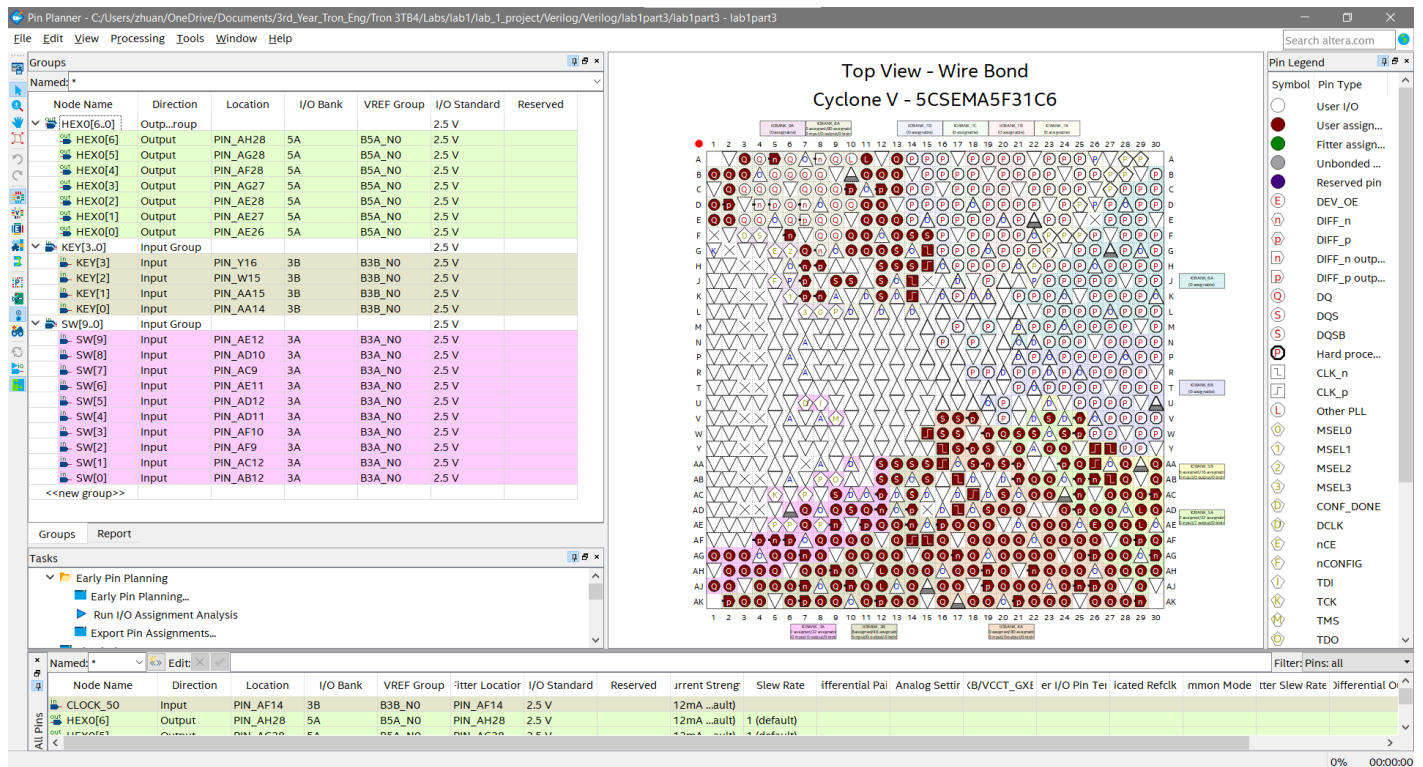


Figure 5: Assignment -> Pin Planner

Questions

In Part 1, we compiled and simulated the modules built during the prelab. We ensured to use various test cases through randomization and observed the output.

In Part 2, we used the multiplexer and switches 0 to 3 to display a specific value on the seven-segment display.

In Part 3, we created a top level module to bring together several other modules, and passed them all through a multiplexer to control what was being output through the seven segment decoder module.

1. The DE1-SoC.qsf file is to map switch, button, key and pin assignments to the corresponding inputs and outputs on the board. These assignments can then be referenced within Verilog to be used as required.
2. Compilation report numbers:
 - a. Total number of logic elements: 24
 - b. Total number of registers: 36
 - c. Total number of pins: 22
 - d. Maximum number of logic elements: 32070

Code

Part 2:

```
module lab1part2 (input [3:0] SW, output [6:0] HEX0);
    seven_seg_decoder decoder(.x(SW), .hex_LEDs(HEX0));
endmodule
```

seven_seg_decoder → Module provided in prelab

Part 3:

```
module lab1part3 (input [9:0] SW, input [3:0] KEY, input CLOCK_50, output [6:0] HEX0);
    wire [3:0] b_cnt;
    wire [29:0] c_cnt;
    wire [3:0] disp_in;

    seven_seg_decoder decoder (.x(disp_in), .hex_LEDs(HEX0));
    counter_button button (.key(KEY[3]), .reset(KEY[0]), .out(b_cnt));
    counter_clock clock (.clk(CLOCK_50), .reset(KEY[0]), .out(c_cnt));
    multiplexer multiplex (.a(SW[3:0]), .b(b_cnt), .c(c_cnt[29:26]),
                          .sel(SW[9:8]), .out(disp_in));
endmodule
```

```
module counter_clock (input clk, reset, output reg[WIDTH-1:0] out);
    parameter WIDTH = 30;
    //2's power of 26 is 67,108,864.
    // that is 1 second (2^26/50e6 = 1.34), if count is using CLOCK 50
    always@(posedge clk or negedge reset) begin
        if(!reset) begin
            out <= 30'b0;
        end else begin
            out <= out + 1'b1;
        end
    end
endmodule
```

```
module counter_button (input key, reset, output reg [3:0] out);
    always @(negedge key or negedge reset) begin
        if (!reset)
            out <= 4'b0;
        else
            out <= out + 1'b1;
        end
    end
endmodule
```

```

module multiplexer (input [3:0] a, b, c, input [1:0] sel, output reg [3:0] out);
    always @(a or b or c or sel) begin
        case (sel)
            2'b00: out <= a;           // Decoder
            2'b01: out <= b;           // Button Counter
            2'b10: out <= c;           // Clock Counter
            2'b11: out <= 4'b1111;    // OFF
        endcase
    end
endmodule

```

```

module seven_seg_decoder(input [3:0] x, output [6:0] hex_LEDs);
    reg [6:0] reg_LEDs;
    assign hex_LEDs[0]= ~x[3] & ~x[2] & ~x[1] & x[0] |
        ~x[3] & x[2] & ~x[1] & ~x[0] |
        x[3] & x[2] & x[0] |
        x[3] & x[1] & x[0];    /* expression for segment 0 */

    assign hex_LEDs[1]=  x[2] & ~x[1] & x[0] |
        x[3] & x[2] & x[0] |
        x[2] & x[1] & ~x[0] |
        x[3] & x[1] & ~x[0];    /* expression for segment 1 */

    assign hex_LEDs[6:2]=reg_LEDs[6:2];

    always @(*)
    begin
        case (x)
            4'b0000: reg_LEDs[6:2]=5'b10000; //7'b1000000 decimal 0
            4'b0001: reg_LEDs[6:2]=5'b11110; //7'b1111001 decimal 1
            4'b0010: reg_LEDs[6:2]=5'b01001; //7'b0100100 decimal 2
            4'b0011: reg_LEDs[6:2]=5'b01100; //7'b0110000 decimal 3
            4'b0100: reg_LEDs[6:2]=5'b00110; //7'b0011001 decimal 4
            4'b0101: reg_LEDs[6:2]=5'b00100; //7'b0100100 decimal 5
            4'b0110: reg_LEDs[6:2]=5'b00000; //7'b0000010 decimal 6
            4'b0111: reg_LEDs[6:2]=5'b11110; //7'b1111000 decimal 7
            4'b1000: reg_LEDs[6:2]=5'b00000; //7'b0000000 decimal 8
            4'b1001: reg_LEDs[6:2]=5'b00100; //7'b0010000 decimal 9
            4'b1010: reg_LEDs[6:2]=5'b00100; //7'b0010010 decimal S
            4'b1011: reg_LEDs[6:2]=5'b00010; //7'b0001001 decimal H
            4'b1100: reg_LEDs[6:2]=5'b00010; //7'b0001000 decimal A
            4'b1101: reg_LEDs[6:2]=5'b01010; //7'b0101011 decimal N
            4'b1110: reg_LEDs[6:2]=5'b10000; //7'b1000010 decimal G
            4'b1111: reg_LEDs[6:2]=5'b11111; //7'b1111111 ALL OFF
        endcase
    end
endmodule

```

